

Project 2:-

Simulate a full wave rectifier.


Infer its behaviour and explain its rectification efficiency and its ripple factor in comparison to half wave rectifier.


Group member name :- Ravi Prakash Yadav

Prabal Singh


Shivam Giri

Rishav Raj

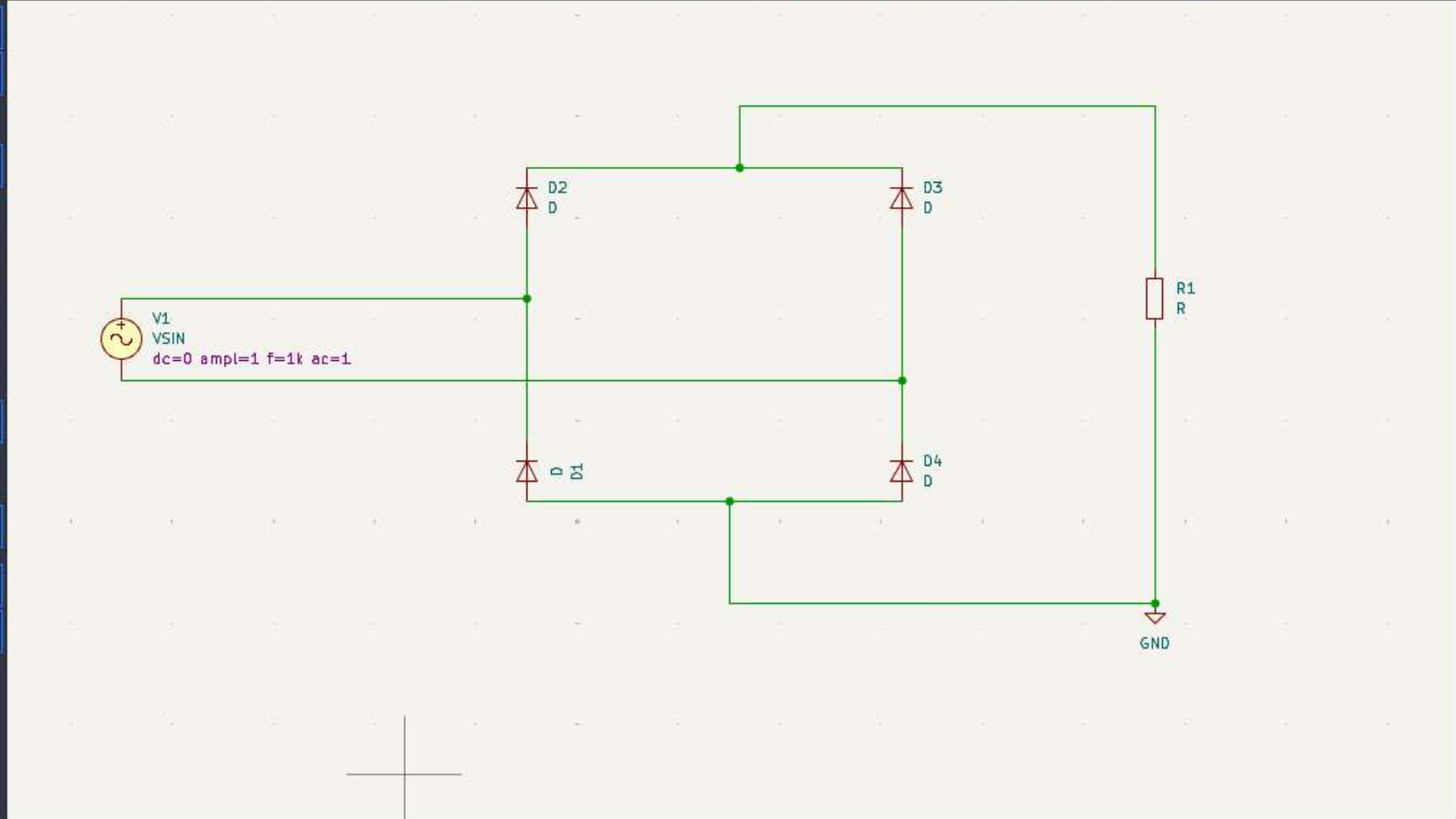

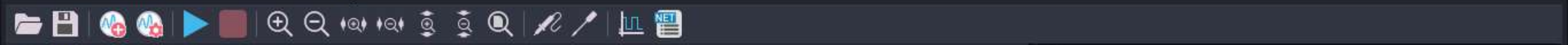

Analysis 1 - TRAN

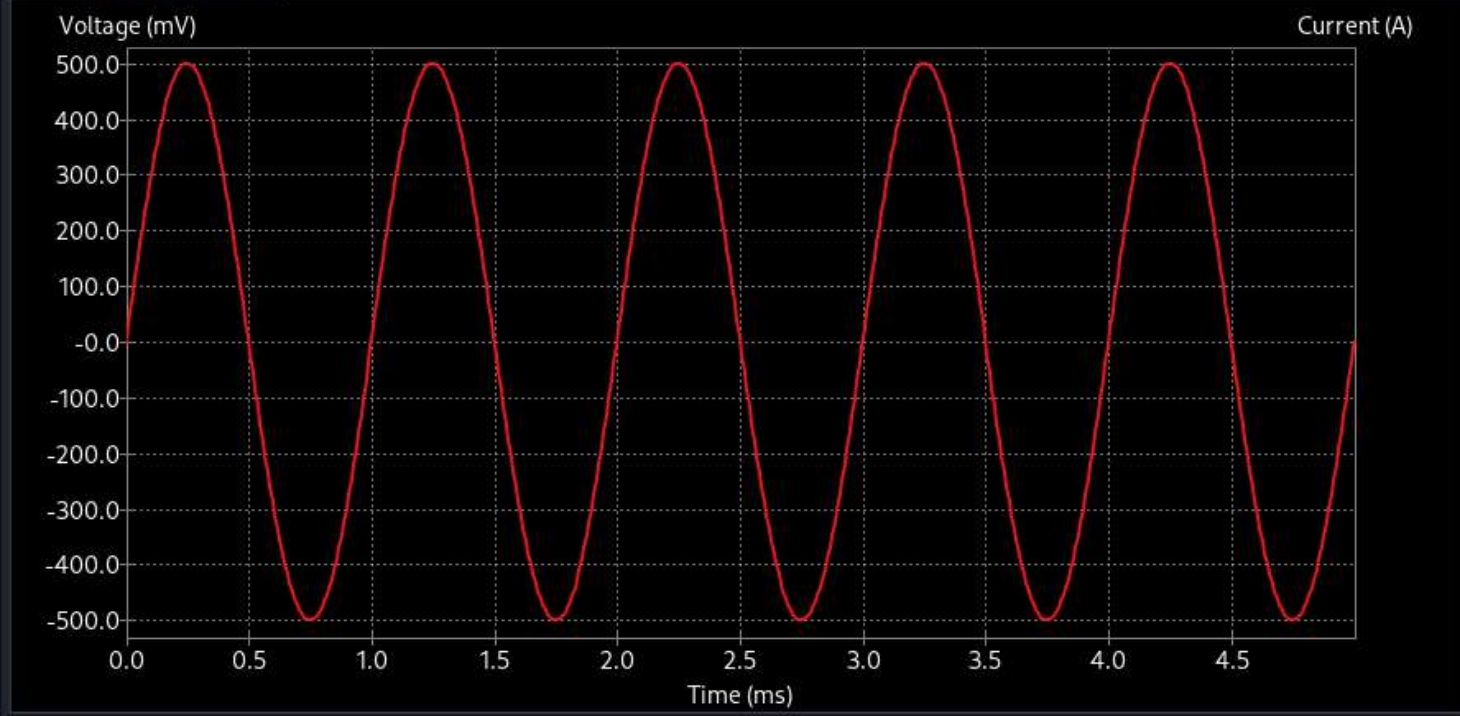

Circuit: KiCad schematic
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Using SPARSE 1.3 as Direct Linear Solver
Warning: r1: resistance too low or not given, set to 1 mOhm
Operating point simulation skipped by 'uic',
now using transient initial conditions.
Reference value : 1.000000e-08
No. of Data Rows : 515

Filter

Signal	Plot	Color	Cursor 1	Cursor 2
V(Net_D1-K_)	<input checked="" type="checkbox"/>	Red	<input type="checkbox"/>	<input type="checkbox"/>
V(Net_D2-K_)	<input type="checkbox"/>		<input type="checkbox"/>	<input type="checkbox"/>
V(Net_D3-A_)	<input type="checkbox"/>		<input type="checkbox"/>	<input type="checkbox"/>
I(D1)	<input type="checkbox"/>		<input type="checkbox"/>	<input type="checkbox"/>
I(D2)	<input type="checkbox"/>		<input type="checkbox"/>	<input type="checkbox"/>
I(D3)	<input type="checkbox"/>		<input type="checkbox"/>	<input type="checkbox"/>
I(D4)	<input type="checkbox"/>		<input type="checkbox"/>	<input type="checkbox"/>
I(R1)	<input type="checkbox"/>		<input type="checkbox"/>	<input type="checkbox"/>
I(V1)	<input type="checkbox"/>		<input type="checkbox"/>	<input type="checkbox"/>
P(D1)	<input type="checkbox"/>		<input type="checkbox"/>	<input type="checkbox"/>

Cursor	Signal	Time (ms)	Value


Measurement	Value

* [Unsaved] — SPICE Simulator

File View Simulation Preferences Help



Analysis 1 - TRAN

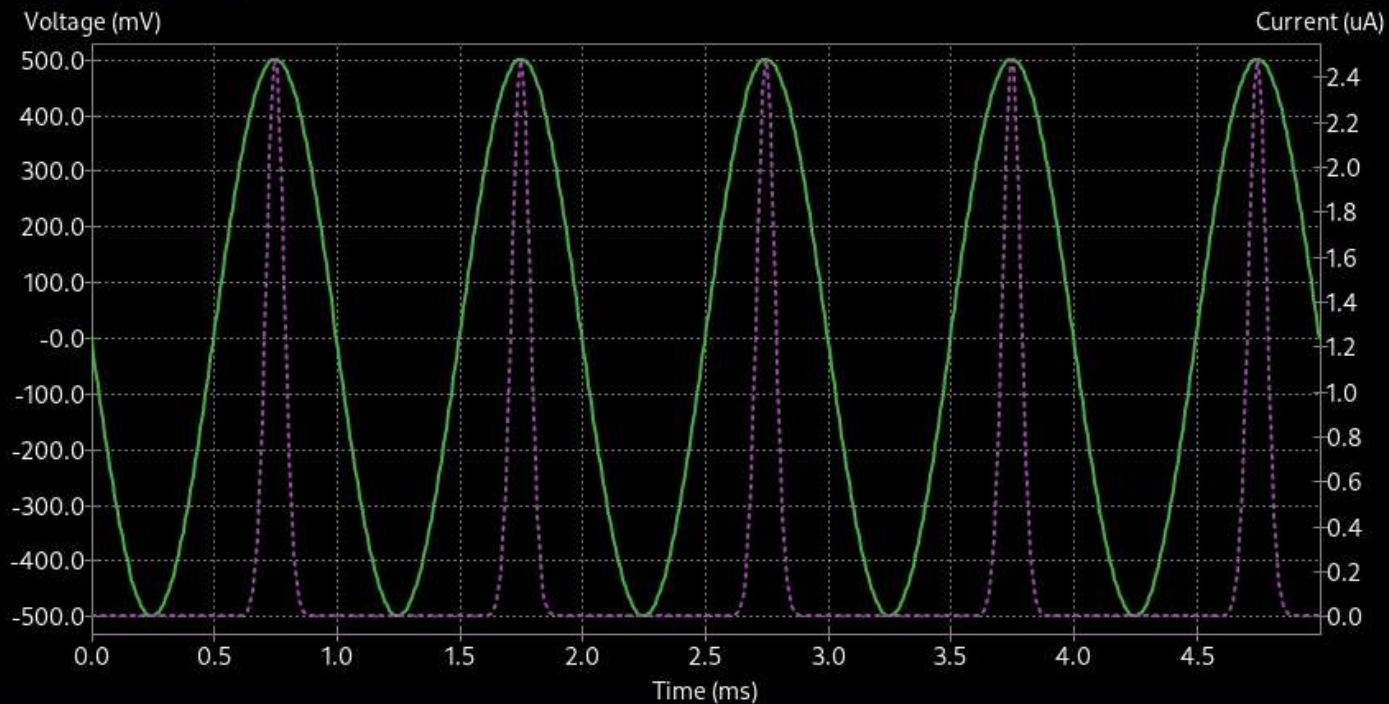


Filter

Signal	Plot	Color	Cursor 1	Cursor 2
V(Net_D1-K_)	<input type="checkbox"/>		<input type="checkbox"/>	<input type="checkbox"/>
V(Net_D2-K_)	<input type="checkbox"/>		<input type="checkbox"/>	<input type="checkbox"/>
V(Net_D3-A_)	<input checked="" type="checkbox"/>	Green	<input type="checkbox"/>	<input type="checkbox"/>
I(D1)	<input checked="" type="checkbox"/>	Purple	<input type="checkbox"/>	<input type="checkbox"/>
I(D2)	<input type="checkbox"/>		<input type="checkbox"/>	<input type="checkbox"/>
I(D3)	<input type="checkbox"/>		<input type="checkbox"/>	<input type="checkbox"/>
I(D4)	<input type="checkbox"/>		<input type="checkbox"/>	<input type="checkbox"/>
I(R1)	<input type="checkbox"/>		<input type="checkbox"/>	<input type="checkbox"/>
I(V1)	<input type="checkbox"/>		<input type="checkbox"/>	<input type="checkbox"/>
P(D1)	<input type="checkbox"/>		<input type="checkbox"/>	<input type="checkbox"/>


Cursor	Signal	Time (ms)	Value
--------	--------	-----------	-------

Measurement	Value
-------------	-------

Circuit: KiCad schematic
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Using SPARSE 1.3 as Direct Linear Solver
Warning: r1: resistance too low or not given, set to 1 mOhm
Operating point simulation skipped by 'uic',
now using transient initial conditions.
Reference value : 1.000000e-08
No. of Data Rows : 515

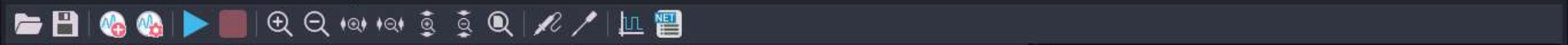

Analysis 1 - TRAN

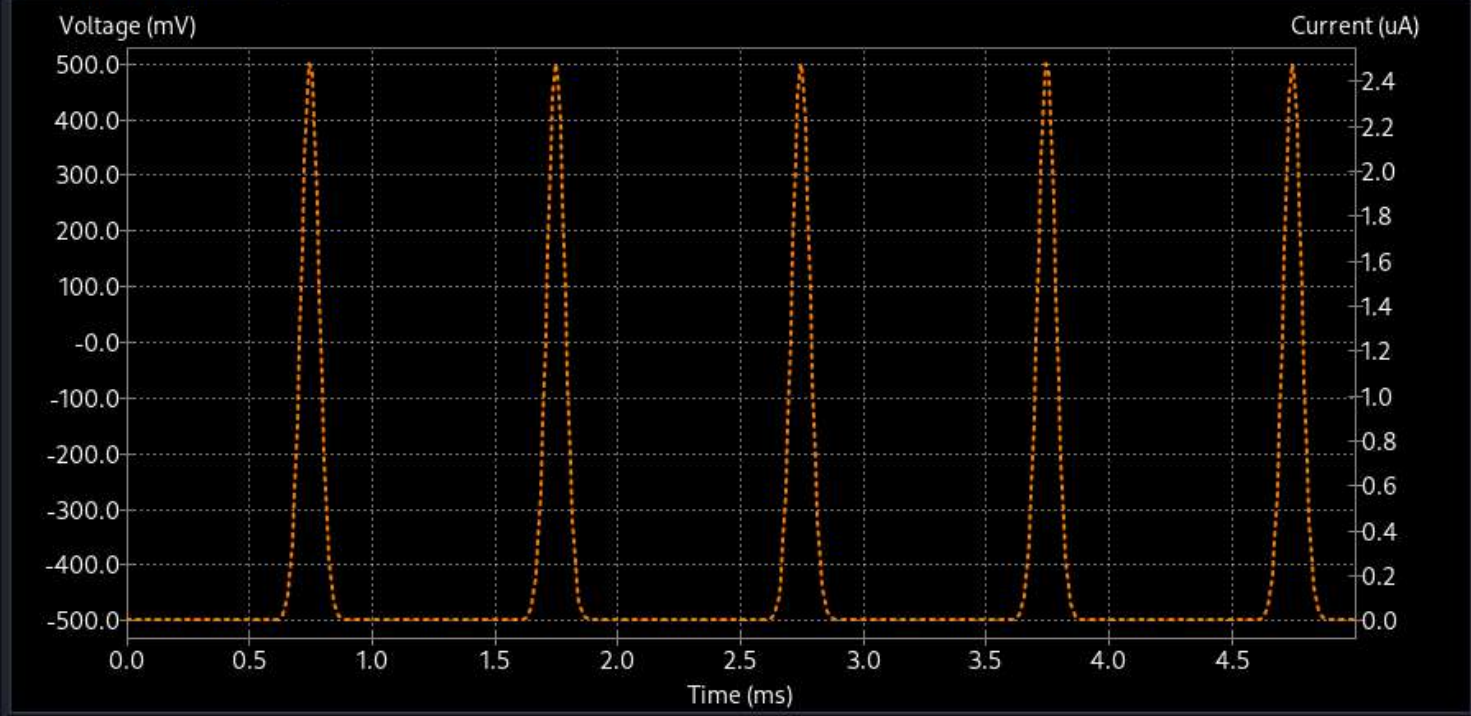

Circuit: KiCad schematic
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Using SPARSE 1.3 as Direct Linear Solver
Warning: r1: resistance too low or not given, set to 1 m0hm
Operating point simulation skipped by 'uic',
now using transient initial conditions.
Reference value : 1.00000e-08
No. of Data Rows : 515

Filter

Signal	Plot	Color	Cursor 1	Cursor 2
V(Net_D1-K_)	<input type="checkbox"/>			
V(Net_D2-K_)	<input type="checkbox"/>			
V(Net_D3-A_)	<input type="checkbox"/>			
I(D1)	<input type="checkbox"/>			
I(D2)	<input type="checkbox"/>			
I(D3)	<input checked="" type="checkbox"/>	Orange	<input type="checkbox"/>	<input type="checkbox"/>
I(D4)	<input type="checkbox"/>			
I(R1)	<input type="checkbox"/>			
I(V1)	<input type="checkbox"/>			
P(D1)	<input type="checkbox"/>			


Cursor	Signal	Time (ms)	Value

Measurement	Value

File View Simulation Preferences Help



Analysis 1 - TRAN

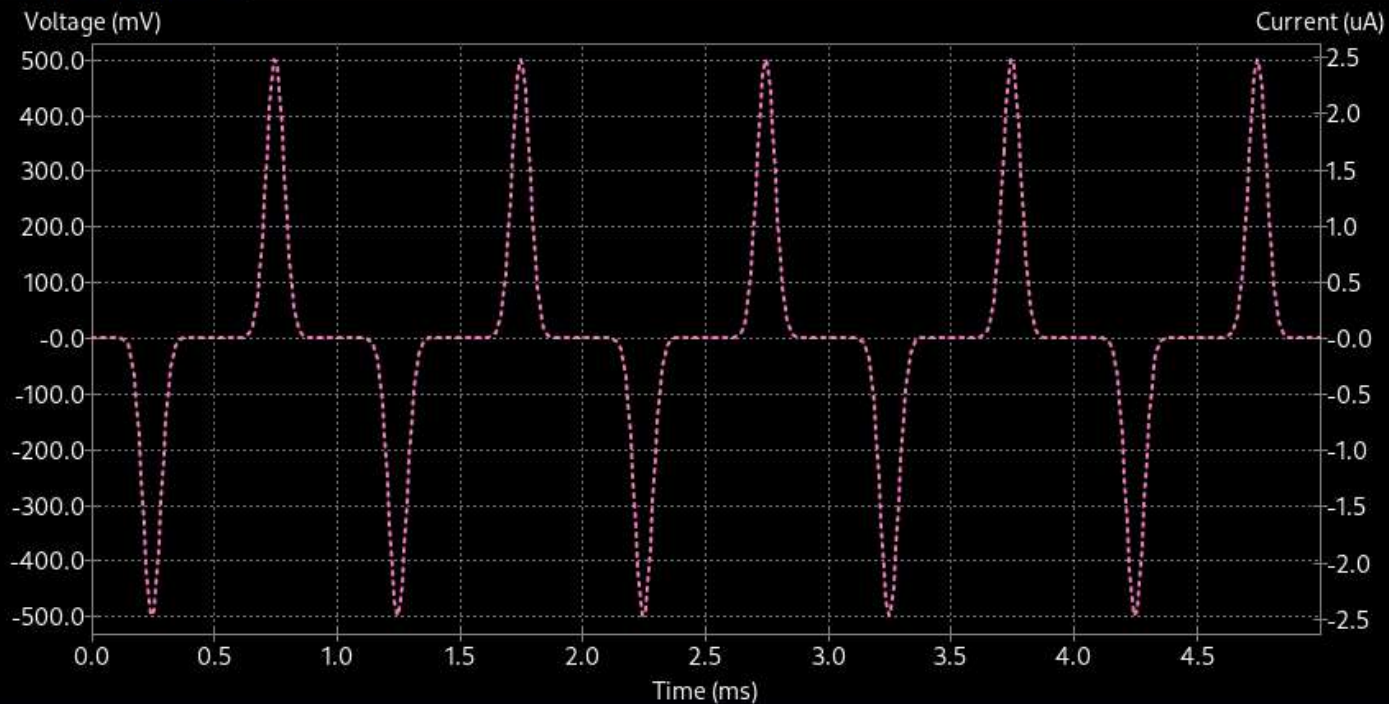

Filter

Signal	Plot	Color	Cursor 1	Cursor 2
V(Net_D1-K_)	<input type="checkbox"/>			
V(Net_D2-K_)	<input type="checkbox"/>			
V(Net_D3-A_)	<input type="checkbox"/>			
I(D1)	<input type="checkbox"/>			
I(D2)	<input type="checkbox"/>			
I(D3)	<input type="checkbox"/>			
I(D4)	<input type="checkbox"/>			
I(R1)	<input type="checkbox"/>			
I(V1)	<input checked="" type="checkbox"/>	pink	<input type="checkbox"/>	<input type="checkbox"/>
P(D1)	<input type="checkbox"/>			

Cursor	Signal	Time (ms)	Value
--------	--------	-----------	-------


Measurement	Value
-------------	-------

Circuit: KiCad schematic
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Using SPARSE 1.3 as Direct Linear Solver
Warning: r1: resistance too low or not given, set to 1 mOhm
Operating point simulation skipped by 'uic',
now using transient initial conditions.
Reference value : 1.000000e-08
No. of Data Rows : 515

File View Simulation Preferences Help



Analysis 1 - TRAN

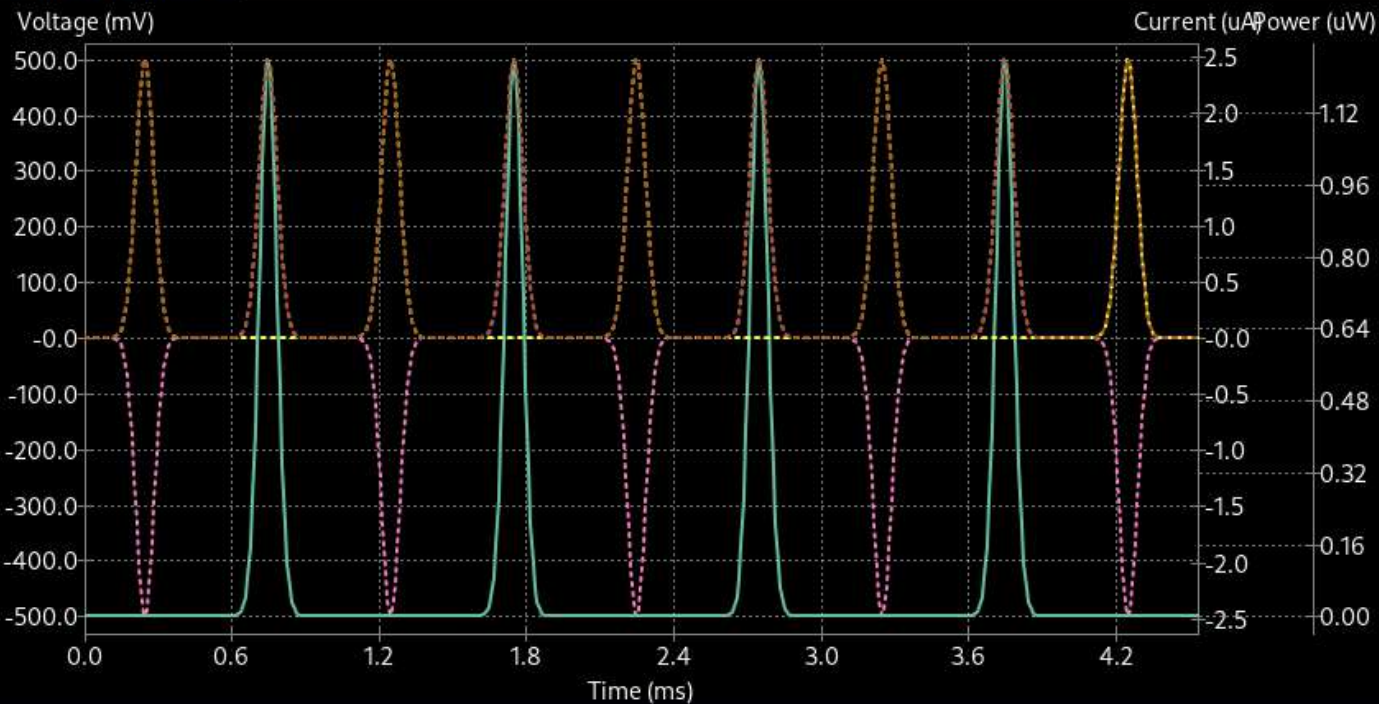

Circuit: KiCad schematic
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Using SPARSE 1.3 as Direct Linear Solver
Warning: r1: resistance too low or not given, set to 1 mOhm
Operating point simulation skipped by 'uic',
now using transient initial conditions.
Reference value : 1.000000e-08
No. of Data Rows : 515

Filter

Signal	Plot	Color	Cursor 1	Cursor 2
V(Net_D1-K_)	<input type="checkbox"/>			
V(Net_D2-K_)	<input type="checkbox"/>			
V(Net_D3-A_)	<input type="checkbox"/>			
I(D1)	<input type="checkbox"/>			
I(D2)	<input type="checkbox"/>			
I(D3)	<input type="checkbox"/>			
I(D4)	<input checked="" type="checkbox"/>			
I(R1)	<input checked="" type="checkbox"/>			
I(V1)	<input checked="" type="checkbox"/>			
P(D1)	<input checked="" type="checkbox"/>			


Cursor	Signal	Time (ms)	Value
--------	--------	-----------	-------

Measurement	Value
-------------	-------

File View Simulation Preferences Help



Analysis 1 - TRAN

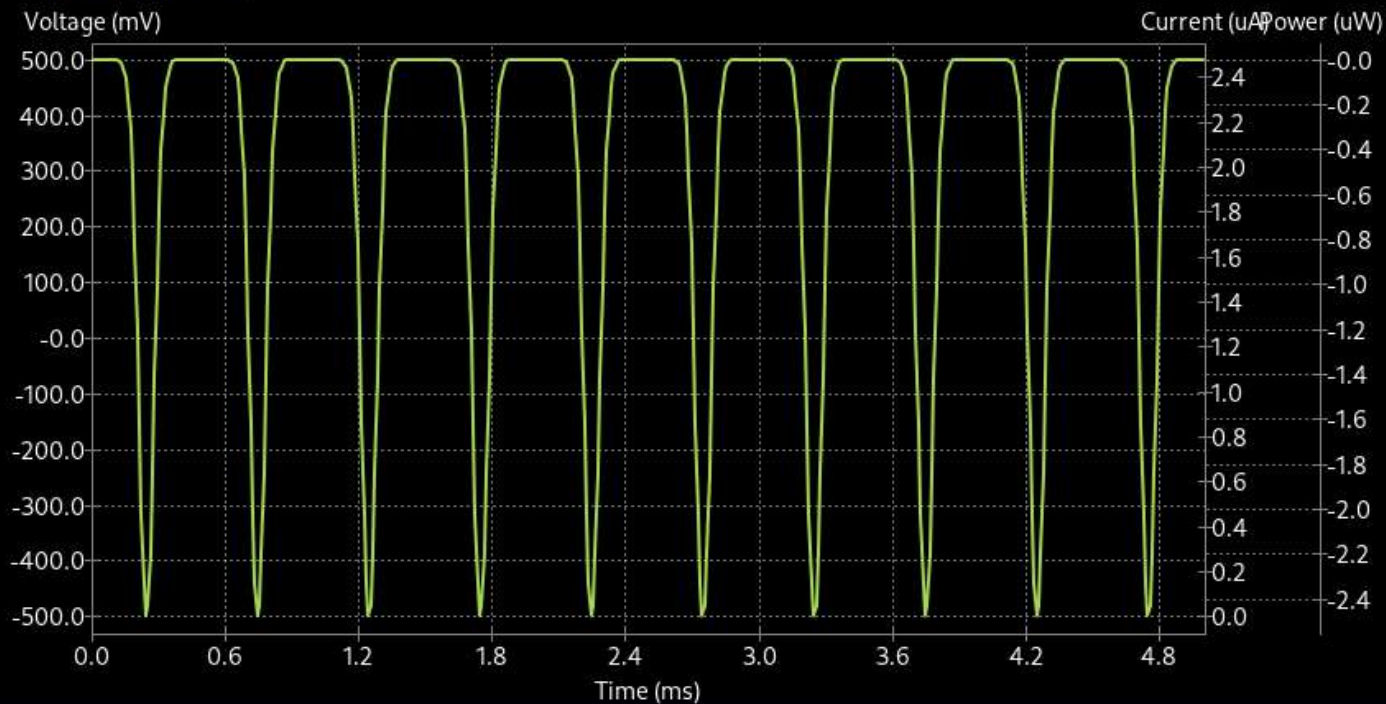

Circuit: KiCad schematic
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Using SPARSE 1.3 as Direct Linear Solver
Warning: r1: resistance too low or not given, set to 1 mOhm
Operating point simulation skipped by 'uic',
now using transient initial conditions.
Reference value : 1.000000e-08
No. of Data Rows : 515

Filter

Signal	Plot	Color	Cursor 1	Cursor 2
I(D3)	<input type="checkbox"/>			
I(D4)	<input type="checkbox"/>			
I(R1)	<input type="checkbox"/>			
I(V1)	<input type="checkbox"/>			
P(D1)	<input type="checkbox"/>			
P(D2)	<input type="checkbox"/>			
P(D3)	<input type="checkbox"/>			
P(D4)	<input type="checkbox"/>			
P(R1)	<input type="checkbox"/>			
P(V1)	<input checked="" type="checkbox"/>			

Cursor	Signal	Time	Value
--------	--------	------	-------

Measurement	Value
-------------	-------

1. Behavior of Full-Wave Rectifier (Bridge Configuration)

During the positive half-cycle of the AC input:

Diodes D2 and D4 conduct.

Current flows through the load resistor R1 in one direction.

During the negative half-cycle:

Diodes D1 and D3 conduct.

Current still flows in the same direction through R1.

Result: Output across the resistor is unidirectional (pulsating DC) with double the frequency of the input AC. If input is 1 kHz, the output ripple is at 2 kHz.

2. Rectification Efficiency (η)

Rectification efficiency is the ratio of DC power delivered to the load to the AC power supplied.

Full-Wave Rectifier Efficiency:

$$\eta = 81.2\%$$

Half-Wave Rectifier Efficiency:

$$\eta = 40.6\%$$

Conclusion:

A full-wave rectifier is twice as efficient as a half-wave rectifier because it utilizes both halves of the AC cycle.

3. Ripple Factor (γ)

Ripple factor measures the amount of AC content in the output DC. Lower is better.

Ripple Factor for Full-Wave Rectifier:

$$\gamma = 0.482$$

Ripple Factor for Half-Wave Rectifier:

$$\gamma = 1.21$$

Conclusion:

The full-wave rectifier produces smoother DC output compared to a half-wave rectifier. You can reduce ripple further by adding a filter capacitor in parallel with the load.